

MATH 214 – QUIZ 2 – SOLUTIONS

Consider an electric circuit containing a capacitor, resistor, and battery. The charge  $Q(t)$  on the capacitor satisfies the equation  $\frac{dQ}{dt} + \frac{Q}{C} = V$ , where  $C$  the capacitance, and  $V$  is the constant voltage supplied by the battery.

- (a) (3 pts.) If  $Q(0) = 0$ , find  $Q(t)$  for any time  $t$  (that is, solve the initial value problem).  
 (b) (2 pts.) Find the limiting value that  $Q(t)$  approaches as  $t \rightarrow \infty$ .

Solution: (a) The equation is separable and can be rewritten  $\frac{dQ}{dt} = V - \frac{Q}{C} = \frac{CV - Q}{C}$  which leads to

$$\begin{aligned} \frac{dQ}{dt} &= \frac{CV - Q}{C} \\ \frac{dQ}{CV - Q} &= \frac{dt}{C} \\ -\ln |CV - Q| &= \frac{t}{C} + k \\ |CV - Q| &= e^k e^{-t/C} \\ CV - Q &= c e^{-t/C} \\ Q &= CV - c e^{t/C} \end{aligned}$$

$Q(0) = 0$  leads to  $c = 1$  so the final solution is  $Q = CV(1 - e^{-t/C})$ .

(b) As  $t \rightarrow \infty$ ,  $e^{-t/C} \rightarrow 0$  so that  $Q(t) \rightarrow CV$  as can be seen from the above solution. It can also be seen from the original equation which has an equilibrium solution of  $Q(t) = CV$ . By looking at the direction field associated with this equation, it follows that  $CV$  is attracting and hence that all solutions converge to  $CV$  in the limit.

Consider an electric circuit containing a capacitor, resistor, and battery. The charge  $Q(t)$  on the capacitor satisfies the equation  $\frac{dQ}{dt} + \frac{Q}{C} = V$ , where  $C$  the capacitance, and  $V$  is the constant voltage supplied by the battery.

- (a) (3 pts.) Suppose that  $Q(0) = Q_0 > 0$  (that is, the capacitor has charge  $Q_0$  when  $t = 0$ ), and that the battery is removed from the system and the circuit closed again (that is, we have set  $V = 0$  in the above equation). Find  $Q(t)$  for any time  $t$  (that is, solve the initial value problem).  
 (b) (2 pts.) Assuming the situation described in part (a), find the time  $T$  at which the charge on the capacitor is  $Q_0/2$ .

Solution: (a) The equation we are solving is  $\frac{dQ}{dt} + \frac{Q}{C} = 0$  or  $\frac{dQ}{dt} = -\frac{Q}{C}$  which leads to

$$\begin{aligned}\frac{dQ}{dt} &= -\frac{Q}{C} \\ \frac{dQ}{Q} &= -\frac{dt}{C} \\ \ln |Q| &= -\frac{t}{C} + k \\ |Q| &= e^k e^{-t/C} \\ Q &= c e^{-t/C}\end{aligned}$$

$Q(0) = Q_0$  leads to  $c = Q_0$  so the final solution is  $Q = Q_0 e^{-t/C}$ .

(b) We must solve  $Q_0/2 = Q_0 e^{-T/C}$  which leads to a solution of  $T = C \ln(2)$ .

---

Consider an electric circuit containing a capacitor, resistor, and battery. Suppose that the charge  $Q(t)$  on the capacitor satisfies the equation  $\frac{dQ}{dt} + \frac{Q}{C} = V$ , where  $C$  the capacitance, and  $V$  is the constant voltage supplied by the battery.

- (a) (3 pts.) Suppose that  $C = .10$  farad, and  $V = 10$  volts. If  $Q(0) = 0$ , find  $Q(t)$  for any time  $t$  (that is, solve the initial value problem).
- (b) (2 pts.) Find the time  $T$  required for the charge  $Q$  on the capacitor to reach .50 coulomb.

Solution: (a) The equation we are solving is  $\frac{dQ}{dt} + \frac{Q}{.1} = 10$  or  $\frac{dQ}{dt} = 10 - 10Q$ . This equation is separable and solving it leads to

$$\begin{aligned}\frac{dQ}{dt} &= 10(1 - Q) \\ \frac{dQ}{1 - Q} &= 10dt \\ -\ln |1 - Q| &= 10t + k \\ |1 - Q| &= e^k e^{-10t} \\ Q &= 1 - c e^{-10t}\end{aligned}$$

$Q(0) = 0$  leads to  $c = 1$  so the final solution is  $Q = 1 - e^{-10t}$ .

(b) We must solve  $.50 = 1 - e^{-10T}$  which leads to a solution of  $T = \ln(2)/10$ .